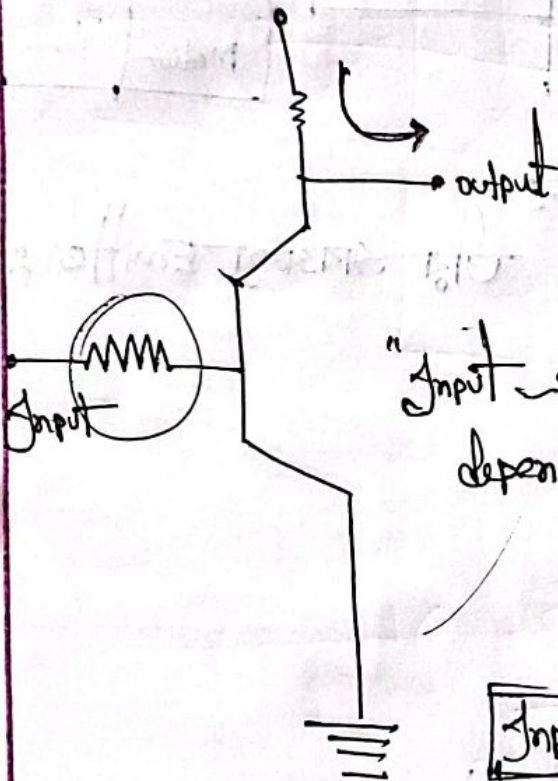


RTL

Register Transistor Logic

Not gate:



"Input is Ground or output depend on it"

Input	output
0	1
1	0