

Operational Amplifier

All question from 5 session

2018-19

3) a. Show the pin ~~diagram~~ configuration of a typical op-amp with its function? - 4

b. Draw the circuit of an op-amp as voltage follower and find an expression for its voltage gain? - 6

c. Draw the circuit for a non inverting amplifier and explain how it works? - 4

4) a. Show the differences between open loop gain and close loop gain? - 3

b. Show the circuit diagram of integrator and differentiator and explain how it works - 6

c. Draw the circuit diagram of subtractor

P.T.O

and explain how it works? - 5 Marks

17-18

3) a. Show the circuit of symbol and terminals of operational amplifier 741C. - 4 Marks

b. Show block diagram for using op-amp in sensor based data acquisition - 4 Marks

c. Draw the circuit for an inverting amplifier.

Deduce the equation of output voltage, current and closed loop gain for inverting amplifier? - 6 Marks
সমীক্ষা (বকরো)

4) a. Explain how an operational amplifier can be used to design voltage follower? - 4 Marks

b. Show the circuit diagram of integrator and differentiator and explain how it works? - 6 Marks

c. What is quantization error? How it is reduced. How an operational amplifier can be used to build inverting adder? - 4 Marks

16-17 Session

3. b. What are differences between open loop gain and close loop gain of operation amplifier? - 3 Marks

c. Show how can an operational amplifier be used as an adder and subtractor? - 6 Marks

4) a. Explain how an operational amplifier be used as an integrator? - 5 Marks

5(b) $\rightarrow$ b. Explain how an op-amp can be used as voltage follower? - 4 Marks

9(b) $\rightarrow$ b. Show how a low pass filter is designed using the operational amplifier? - 5 Marks

25/11/20

c. How voltage gain is obtained for inverting amplifier? - 4 Marks

5) a. Show the circuit diagram of a multichannel amplifier. Show the output voltage analysis and circuit diagram of differentiator.

= 6 Marks

b. Explain how op-amp can be used as voltage follower? - 9 Marks

c. Give the examples where D/A and

A/D converters are used? - 9 Marks

Mix from AD/DA

2015-16 Session

3. a. Write down the characteristics of

ideal op-amp? - 3 Marks

b. What is open loop gain and closed loop gain? Show the pin configuration of a typical op-amp? - 5 Marks

c. How output voltages are calculated for

A.T.O

The circuit of i) non inverting amplifier
ii) summing - 6 Marks

4) a. How cascaded op-amp circuit is designed?

How output voltage is obtained in cascaded op amp circuit? - 2 Marks

b. Design an op-amp circuit with inputs V_1 and V_2 such that $V_o = -2V_1 + 3V_2$ - 4 Marks

c. How voltage gain is obtained for inverting amp? - 3 Marks

5) a) Show the output voltage analysis and circuit diagram for differentiator? - 5 Marks

b. Explain why capacitor and inductor are very useful in electronic circuit? - 9 Marks

Maybe!!!

c. Design an analog computer circuit to solve the differential equation?

$$\frac{d^2}{dt^2} v_o + 3 \frac{d}{dt} v_o + 2v_o = 4 \text{ for } t > 0$$

subject to $v_o(0) = ?$, $v_o'(0) = 0$ → Marks 5
 Asst new type question

2011-12 session

No question from op-amp!!!

2012-13 session

9) a. What is an operational amplifier?

What are the fundamental differences between ideal and practical opamp (Model 2910)

- 9 Marks

← b. Solve the differential equation using appropriate circuit diagram?

$$D^2y + 4Dy + 6y = -5 \text{ volts where } D = \frac{d}{dt}$$

- 4 marks

c. write short notes on i) op-amp as a substrate

ii) Frequency

scaling

iii) Schmitt trigger.

-6 Marks

13-14 session

1.a. what is an operational amplifier?

"The inverting amplifier provides a constant voltage gain with 180 phase shift" - Justify the statement with circuit diagram → 5 Marks


b. Define slew rate and active device solve the differential equation using app. - clt: -

dia -

$$D^2 y + 90 y + 6 D y - 8 y = - f(t) \text{ volts}$$

where $D = \frac{d}{dt}$ - 5 Marks

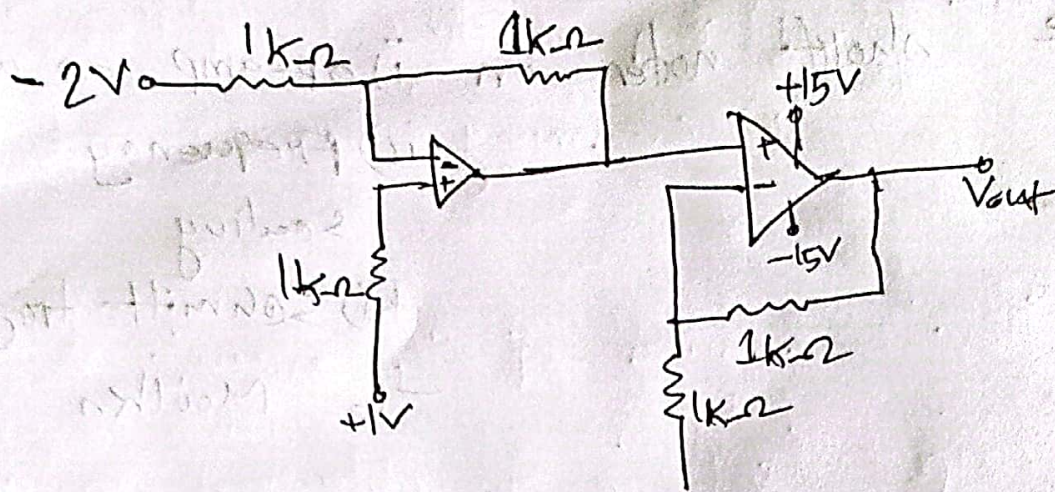c. calculate the output voltage (V_{out}) for the circuit of fig 4(c)



5(b) Sketch the equivalent circuit of ideal op-amp. Suppose for a non inverting amp, the equivalent circuit of

op-amp is shown in fig

5(b)

i) find V_s/V_{out} for $R_{in} = 100k\Omega$

ii) V_s/V_{out} for an ideal op-amp

