

23.11.25

৩৩শিদি স্যাক



gate $\rightarrow$ mosfet, diode,

* Memory $\leftarrow$ Register $\leftarrow$ flipflop $\leftarrow$ gate.

* Micro chip $\rightarrow$ LSI
MSI

* chip design company (bangladeshi, bideshi)

* Sensor $\rightarrow$ How they work

↓
কিভাবে বানানো হয়? $\rightarrow$ how to design


* why digital electronics need for CSE student

* Soil $\rightarrow$ specific meteparameter কিসের উপর নির্ভর করে
কিসের sensor থেকে


* How signal transfer? $\left\{ \begin{array}{l} \text{analog} \\ \text{digital} \end{array} \right.$

* diode/transistor কিভাবে কাজ করে
(work)




* ohms, k Ω , M Ω ,

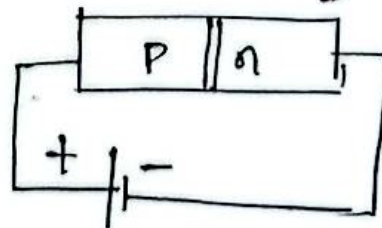

* transistor (use) switch

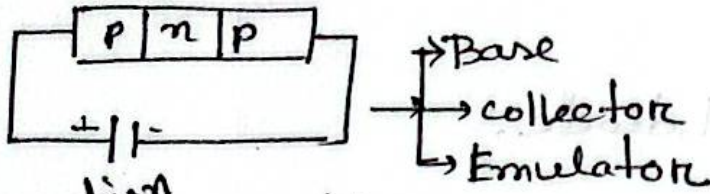

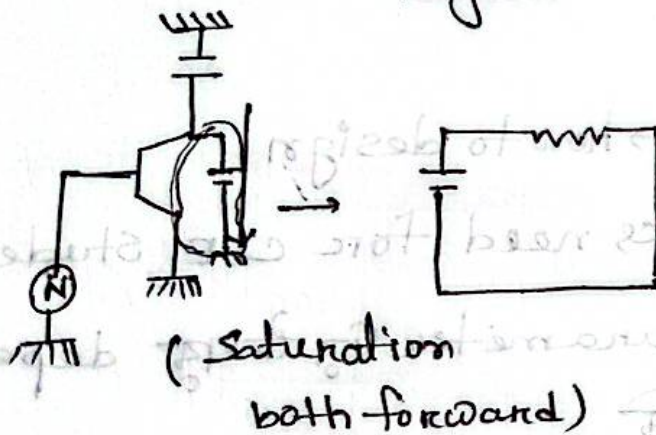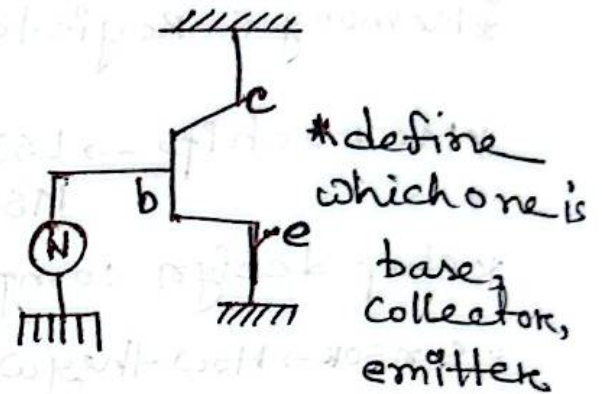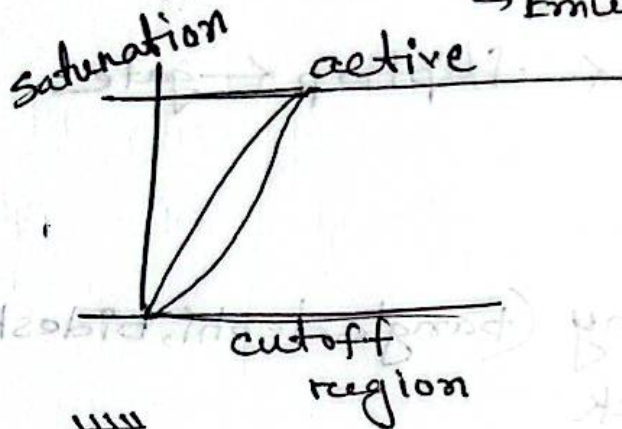Saturation (+, +)
 cutoff (-, -)
 Active (+, -)




* NOR, Nand gate

किछावु ऐकि शव
 (Next class) -

$V_{CC} = 0.2$ (०.२ वोल्ट या २ वोल्ट)



* Technology + Human scycology

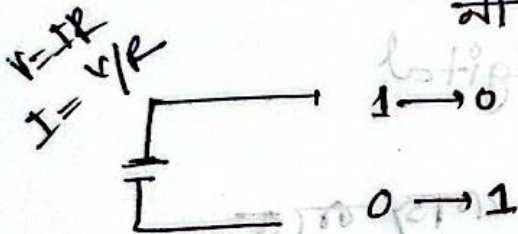

ଆବାର୍ତ୍ତନ କ୍ଷମତା ବିକାଶ frequency allocate କରୁ । TDM
CDM

[Question
ସଂଖ୍ୟା ୧]


୧୫. ୧୨.୨୫
ଡାକ୍ତର ଅମ୍ବୁକା

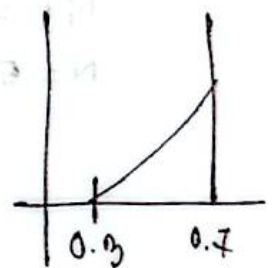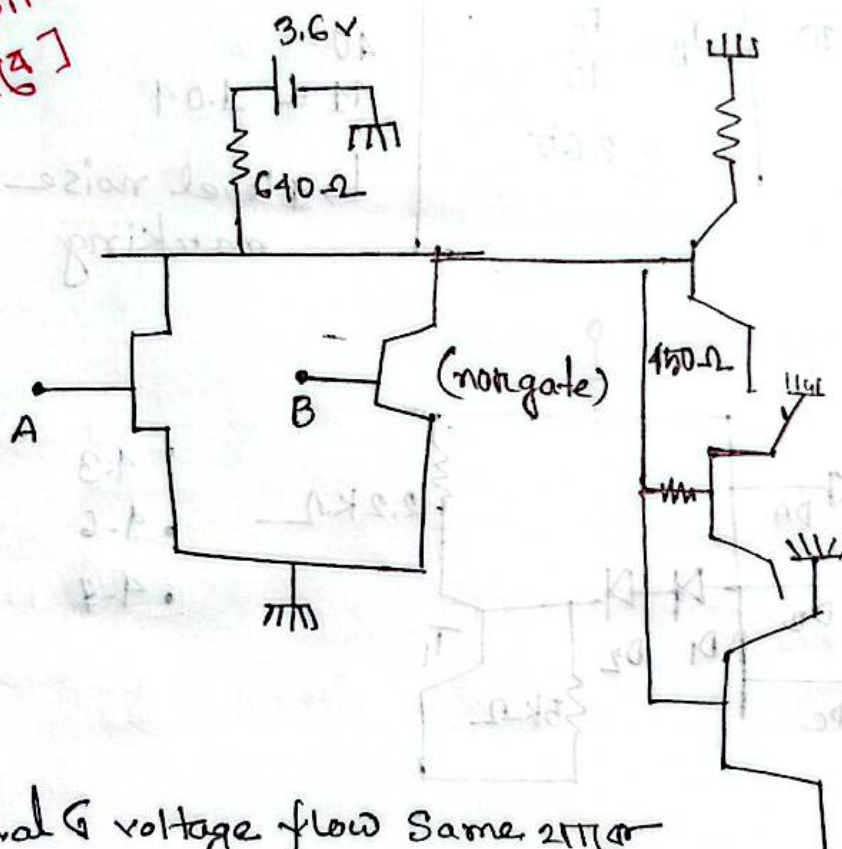

diode
characteristic

Parallel & voltage flow same 211
Series & current flow same 211

*

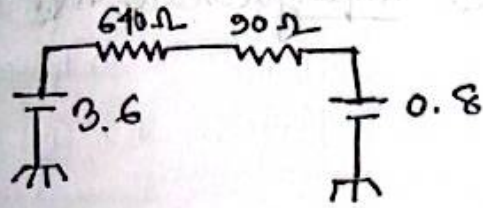

$$\frac{3.6 - 0.8}{610 + 90} = I$$

$$V = IR$$

$$I_C = \frac{3.6 - 0.2}{610}$$

$$HFE, I_B \leq I_C$$

$$HFE = 10$$

$$N = 5$$

$$I_B = \frac{I_C}{10}$$


$$= 2.65$$

$$40 =$$

$$41 = 1.04$$


↳ 1 level noise marking

*

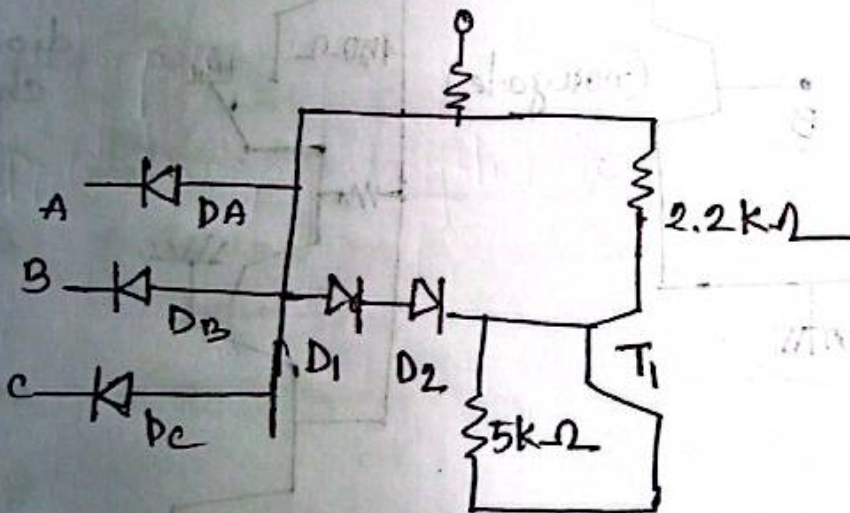


- 4.3
- 4.6
- 4.7



4.1 example)

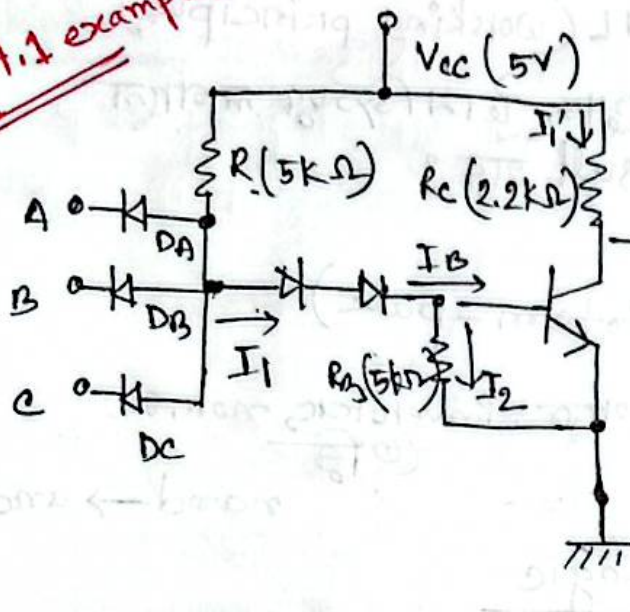

2.12.25

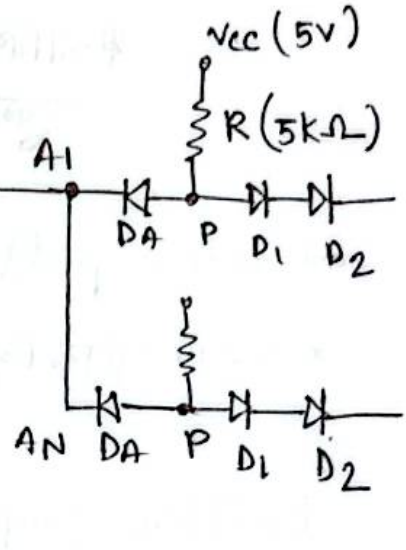

4.8.26
EEE

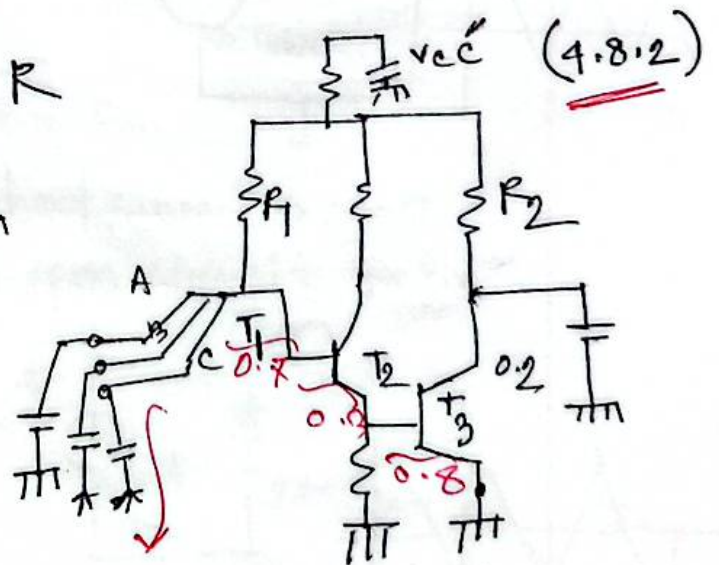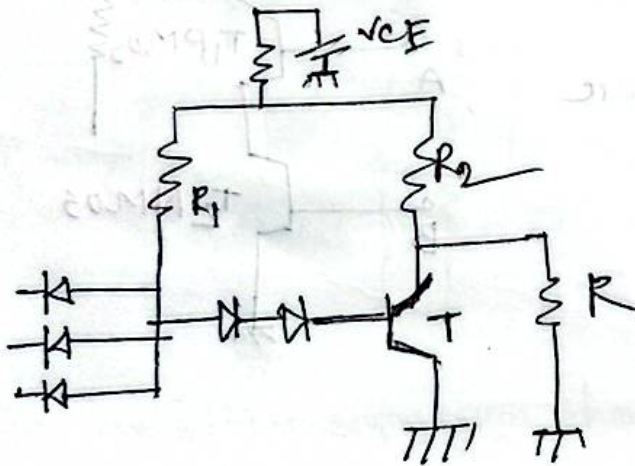

nand gate 63
মতো কাজ করে

* problem of DTL, TTL (working principle)

* આર્કિટેક્ચર, ડ્રોન ડિઝાઇન લાગાલ
કુદરત result શરૂ ?

* active pull up (totem-pole)

* આર્કિટેક્ચર, ડ્રોન ડિઝાઇન, inverter, non, or
નિર્ણય


nand → and

Emitter coupled Logic

CMOS

clamping










operational amplifier

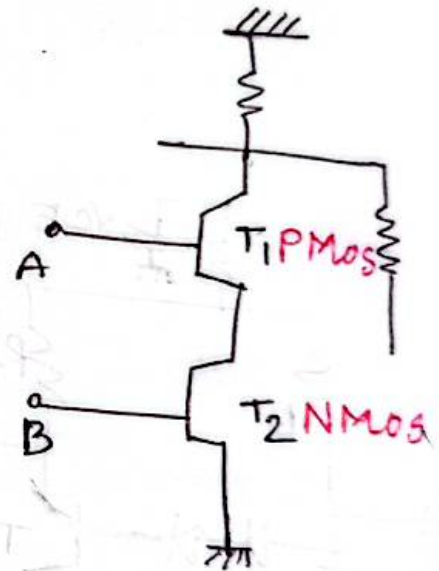



no stop bar


05.01.26

clipper

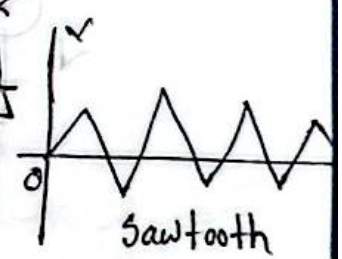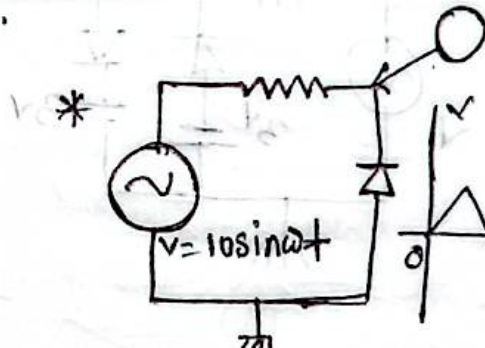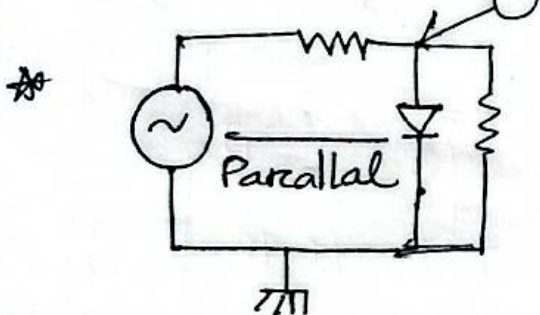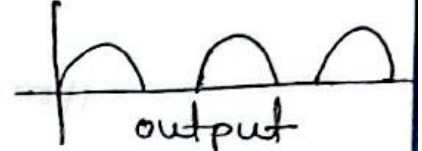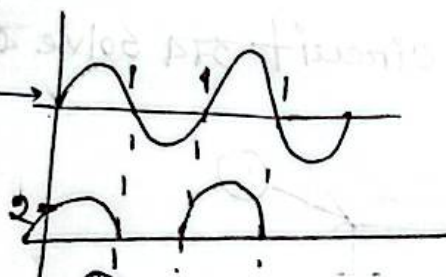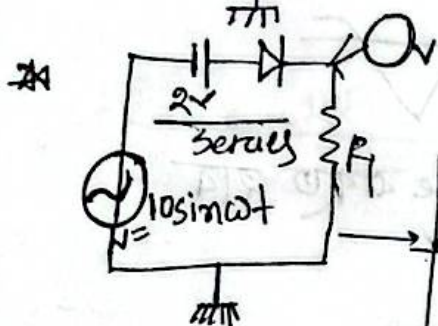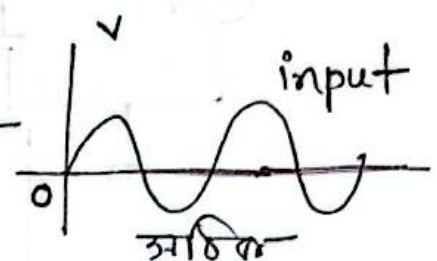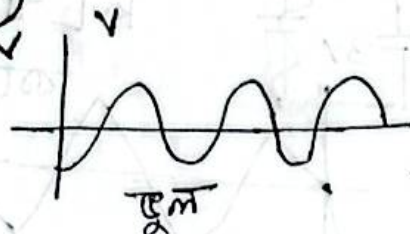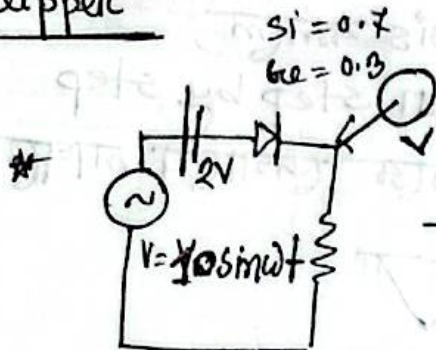

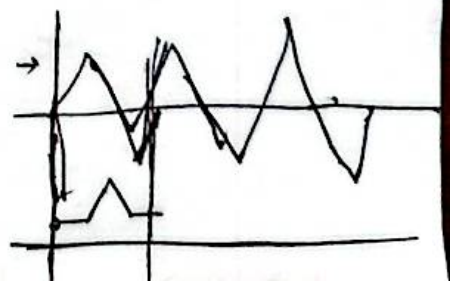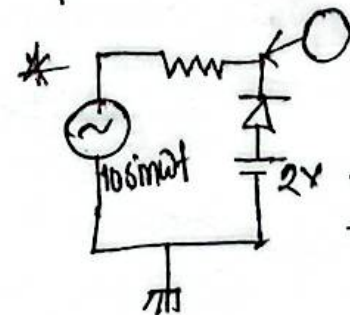
positive output from short circuit $v = 0$
negative output from open circuit $v = v_{in}$



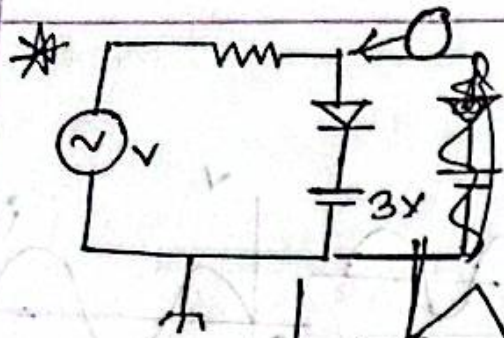



Analysis कमल,
 KVL वा step by step
 करके देखाया जायगा

Homework

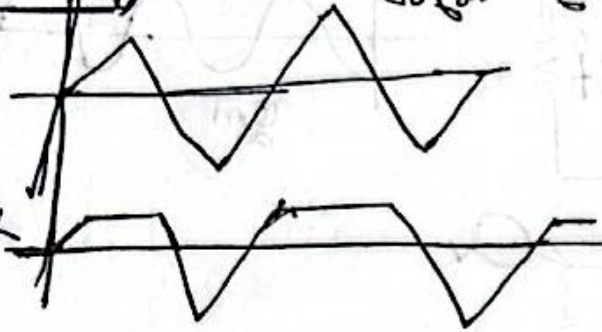

clipper का circuit अब solve करते हैं


Homework

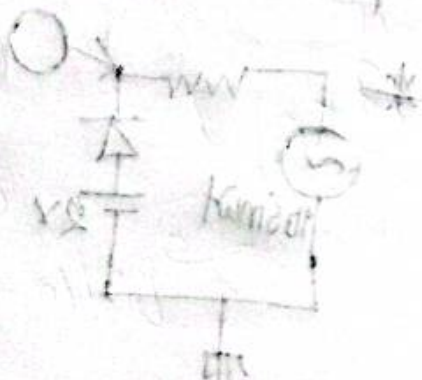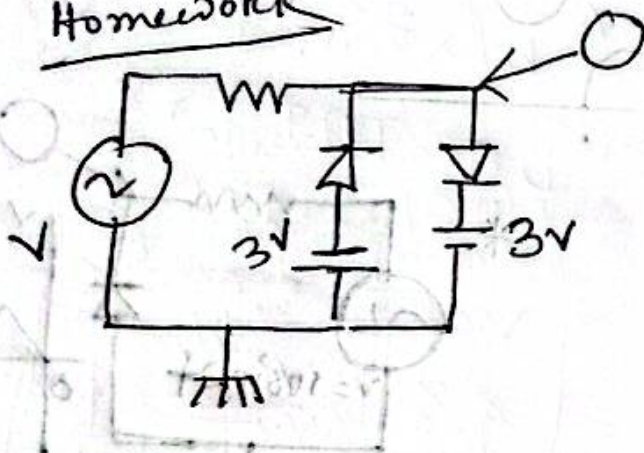

06.01.26

clamping:

Ex-2.24

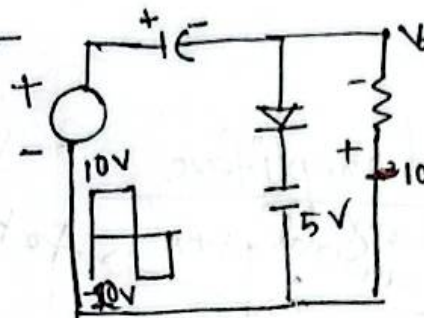


$$10 + V_C - 5V = 0$$

$$V_C = 15V$$

$$+20V + 15 + V_O = 0$$

$$V_O = -35$$

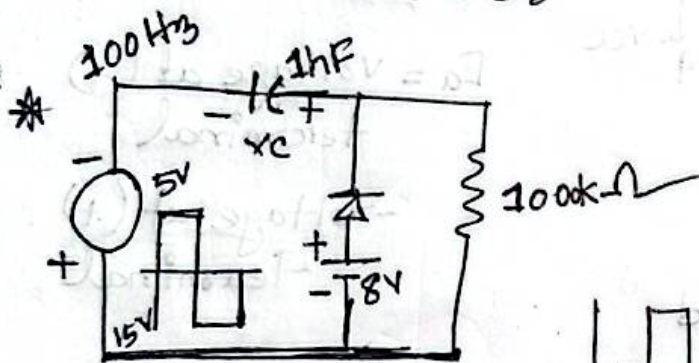


$$+15V - V_C + 8V = 0$$


$$V_C = 23V$$

$$-5V - 23 + V_O = 40$$

$$V_O = 28V$$

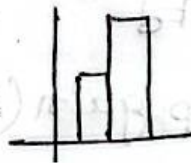


* next class
(operational amplifier)

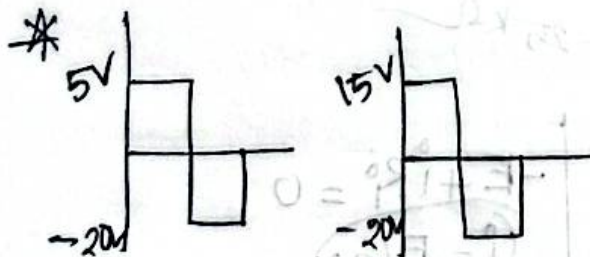

* circuit design

07.01.20

operational amplifiers

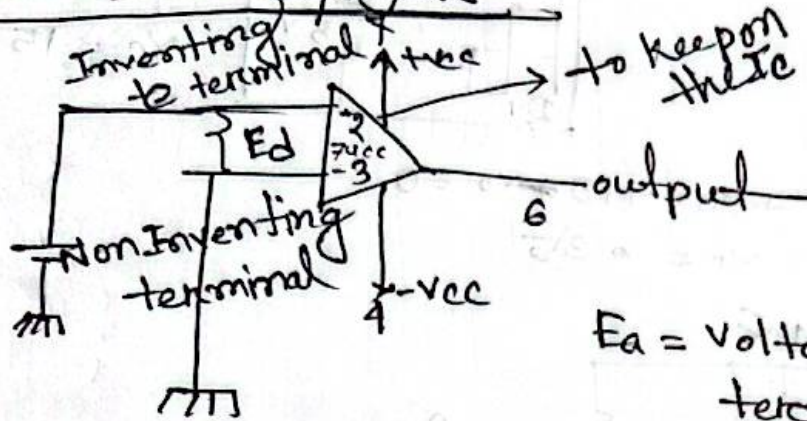


E_d = voltage at (-) terminal
- voltage at (+) terminal

led (10)

$$V_o = A_{ol} \times E_d$$

closed Loop gain (A_{cl})

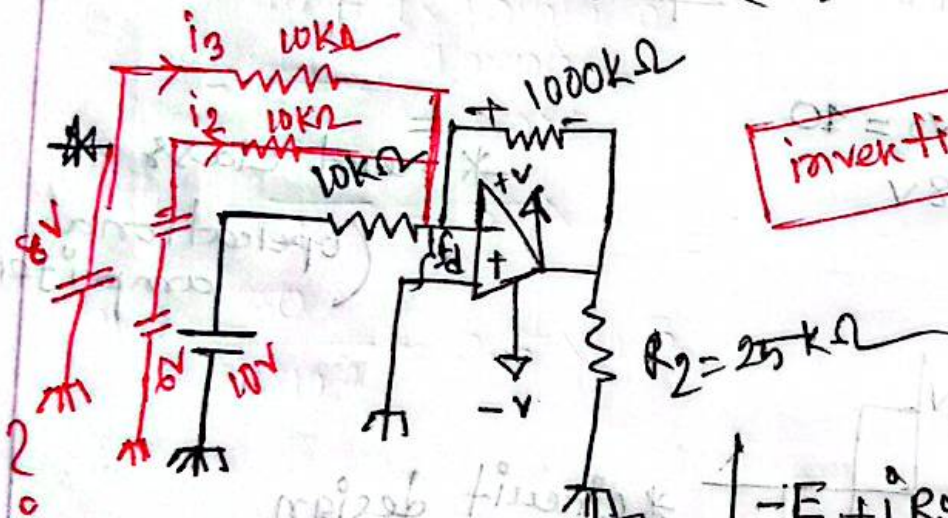

inverting adder

$$V_o = V_{Rf} = -E / R_1 \times R_f$$

output voltage

$$-E + i R_o = 0$$

$$i = E / R_i$$

$$V_{Rf} = i \times R_f$$

$$= E / R_i \times R_f$$

$$\frac{V_o}{E_i} = -\frac{R_f}{R_i} = A_{cl}$$

* $E = 10V$

input current,

V_{Rf}

A_{cl}

V_o

i_L


mathematical question:

* $R_f = 100k\Omega$

$\therefore V_{Rf} = \frac{10V}{10} \times 100k\Omega$

$V_{Rf} = 1000k\Omega$

11.01.26

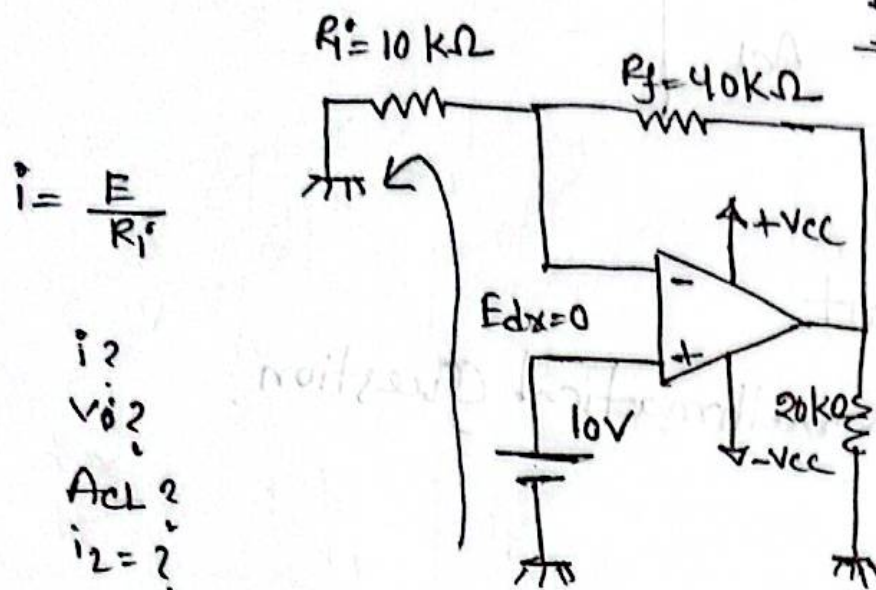

$$i_1 = \frac{E}{R_i}$$

$$i_2 = ?$$

$$V_o = ?$$

$$A_{CL} = ?$$

$$i_L = ?$$

$$V_o = E + V_{Rf}$$

$$= E + i_1 R_f$$

$$= E + \frac{E}{R_i} \times R_f$$

$$= E \left(1 + \frac{R_f}{R_i} \right)$$

$$i_1 = \frac{10}{10 \text{ k}\Omega} = 1 \text{ mA}$$

$$V_o = E + V_{Rf}$$

$$= 10 + (1 \times 40 \times 10^3) \text{ V}$$

$$= 50 \text{ V}$$

$$A_{CL} = \frac{50}{10} = 5$$

$$i_L = \frac{50}{20 \times 10^3} = 2.5 \times 10^{-3}$$


$$A_{CL} = \frac{V_o}{E} = 1 + \frac{R_f}{R_i}$$

সত্য-দুইটি
হল দিলে

$$A_{CL} = 1 + R_f/R_i$$

$$= 1 + 0 = 1$$

*

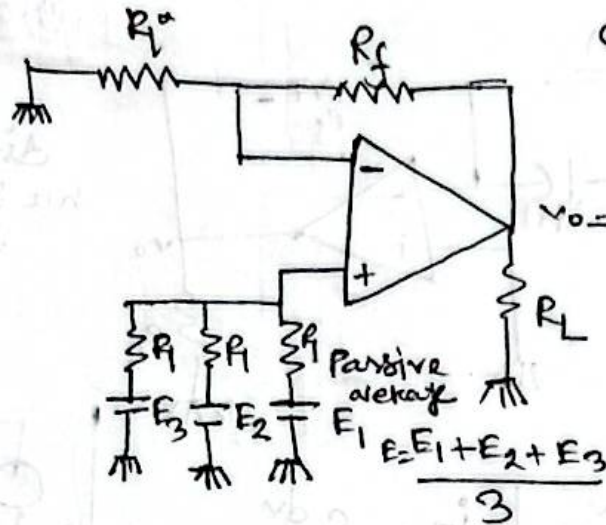


check if the circuit is ok or not?

$$v_0 = E \left(1 + \frac{R_f}{R_i} \right)$$

$$= E \left(1 + \frac{20}{10} \right)$$

यदि E दिले
AF, R_i व
आप 3 गुन
होता

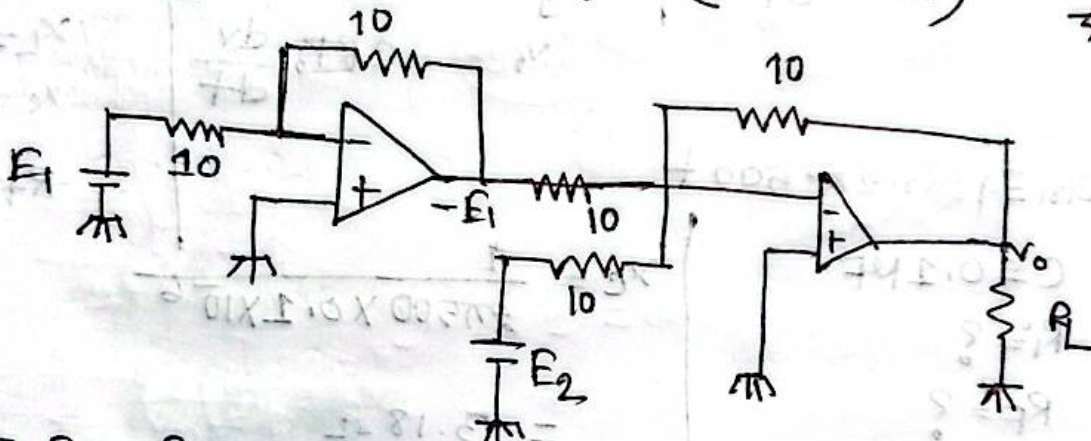* $E_1 - E_2$ (Draw the circuit) → (subtractor)



$$v_0 = E_1 - \frac{R_f}{R_i}$$


$$= -E_1$$

$$v_0 = E_1 + E_2$$

$$v_0 = E_1 + (-E_2)$$

* Differentiation

13.01.20

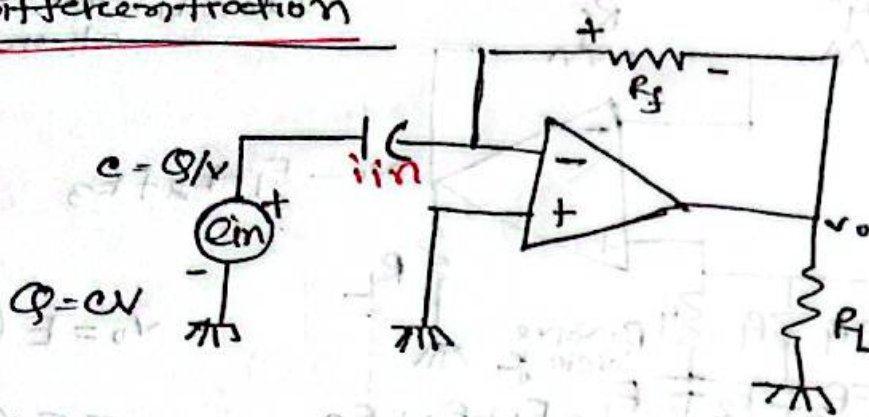

difference
nu signal from
500 to 1000


$$\frac{dQ}{dt} = C \frac{dv}{dt}$$

$$i_{in} = C \frac{dv}{dt}$$

$$i_F = C \frac{dv}{dt}$$

$$-\frac{v_o}{R_f} = C \frac{dv}{dt}$$

$$v_o = -CRF_0 \frac{dv}{dt}$$

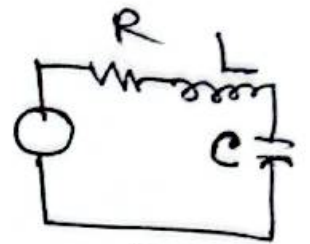

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

$$R + j(X_L - X_C)$$

$$e_{in} = 4 \sin 2\pi 500 t$$

$$C = 0.1 \mu F$$

$$R_i = ?$$

$$R_f = ?$$

$$v_{out} = ?$$

$$X_C = \frac{1}{2\pi 500 \times 0.1 \times 10^{-6}}$$

$$= 3.18 \Omega$$

$$T_1 = \frac{1}{1000}$$

$$T_2 = \frac{1}{1000} [T_2 = 2T_1]$$

$$R_f = \frac{2}{2\pi f C}$$


$$R_i = \frac{1}{2\pi f C}$$

$$X_C = \frac{1}{2\pi f C}$$

~~40~~

$$V_o = -R_f C_i \frac{d e_{in}}{dt} \quad | T_2 = 2 T_1$$

* integrator:

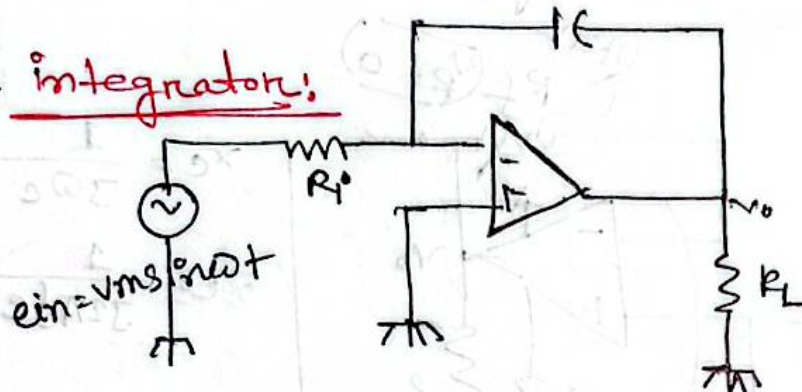

$$i = \frac{e_{in}}{R_i}$$

$$V_c = \frac{Q}{C}$$

$$= \frac{1}{C} \int i \cdot dt$$

$$= \frac{1}{C} \int \frac{e_{in}}{R_i} dt$$

$$= \frac{1}{R_i C} \int e_{in} dt$$

(next topic
filter)

$$V_o = -V_c$$

$$V_o = -\frac{1}{R_i C} \int e_{in} dt$$

$$\frac{V_o}{e_{in}} = \frac{1}{j\omega R_i C} = \frac{1}{j\omega R_i C}$$

$$\frac{V_o}{e_{in}} = \frac{1}{j\omega R_i C}$$


$$\log V_o = \log e_{in} - \log \omega - \log R_i - \log C$$

$$\log V_o = \log e_{in} - \log \omega - \log R_i - \log C$$

$$\log V_o = \log e_{in} - \log \omega - \log R_i - \log C$$

11.01.26

low pulse (non-inverting)

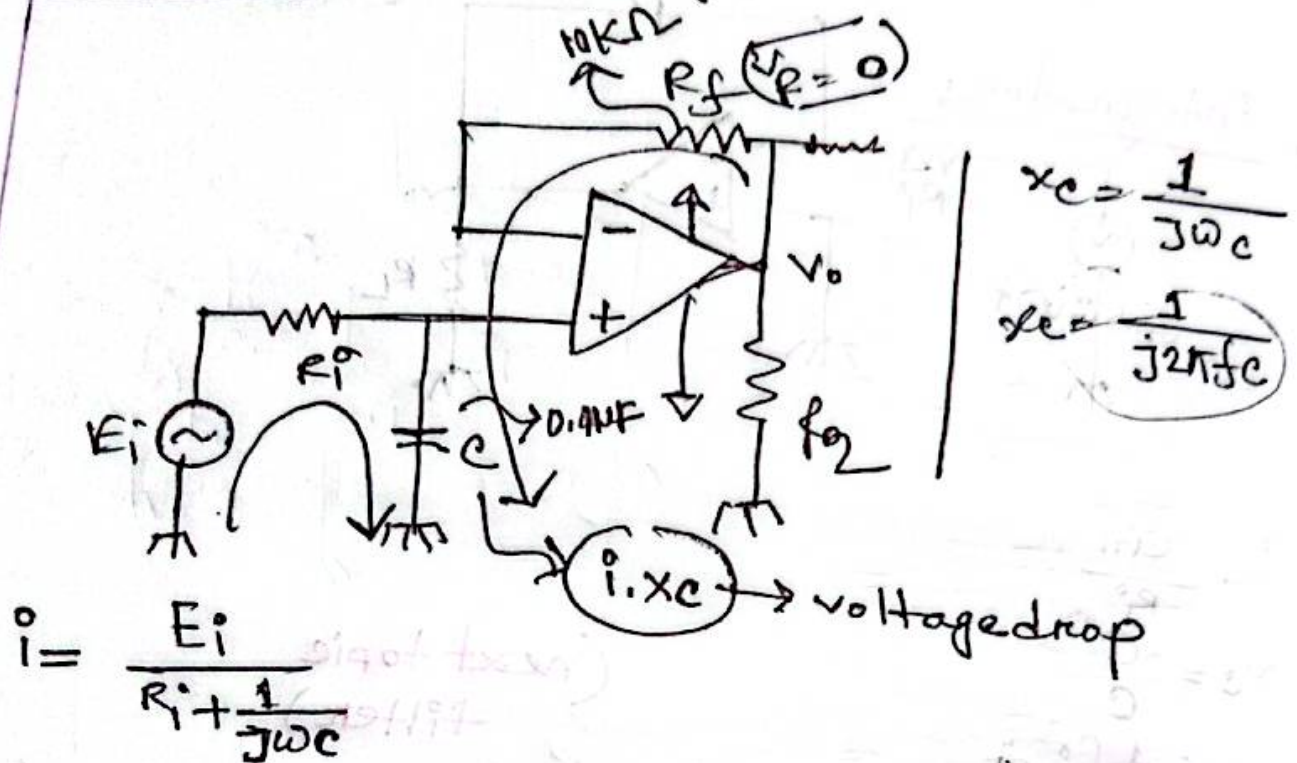

$$V_o = V_c + V_{R_f}$$

$$= V_c = i X_c = \frac{1}{j\omega C} \times \frac{E_i}{R_i + \frac{1}{j\omega C}}$$


$$\therefore A_v = \frac{E_i}{1 + j\omega R C}$$

$$|A_v| = \frac{V_o}{E_i} = \frac{1}{1 + j\omega R C}$$

$|A_v| = 1$ when input = output

$|A_v| = 0$ when input $\neq$ output

$|A_v| < 0$ 1 input $\neq$ output

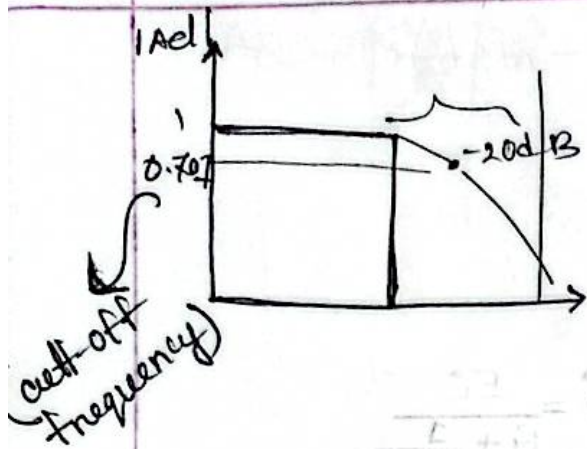

* cutoff frequency f_c ω_c .

$$R = X_C \quad [\omega RC = 1]$$

$$R = \frac{1}{\omega C}$$

$$\omega = \frac{1}{RC}$$

$$\omega_c = \frac{1}{10 \times 10^3 \times 0.04 \times 10^{-6}}$$

* Circuit design করতে হবে * $f_c = 10 \text{ KHz}$.

Circuit draw করে Resistance তার হবে

inductor দিয়ে Circuit draw করতে হবে


$$\left(\frac{1}{\omega C} \right) \sin \omega t$$

$$V + \sin \omega t$$

$$\left(\frac{1}{\omega C} \right) \sin \omega t = V$$

18.01.26

high-pulse

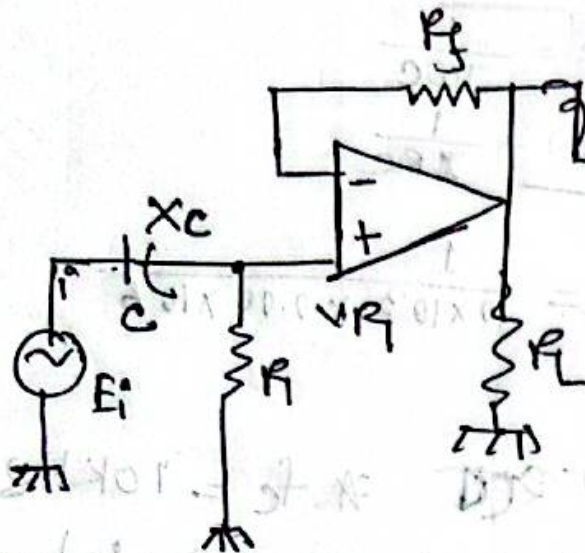

$$i = \frac{E_i}{R + \frac{1}{j\omega C}}$$

$$V_R = \frac{R \times E_i}{R + \frac{1}{j\omega C}}$$

$$= \frac{E_i}{1 + \frac{1}{j\omega RC}}$$

$$= \frac{E_i}{1 - \frac{j}{\omega RC}}$$

$$V_R = \frac{E}{1 - \frac{j}{\omega RC}}$$

$$V_R = \frac{E_i}{1 - j \left(\frac{1}{\omega RC} \right)}$$


$$V_i = V_{Rj} + V_R$$

$$\therefore V_R = \frac{E_i}{1 - j \left(\frac{1}{\omega RC} \right)}$$

$$A_{cl} = \left| \frac{V_o}{R_i} \right| = \frac{1}{1 - j \left(\frac{1}{\omega RC} \right)}$$

$$A_{cl} = \left| \frac{V_o}{R_i} \right|$$

$$20 \log \frac{P_{out}}{P_{in}}$$

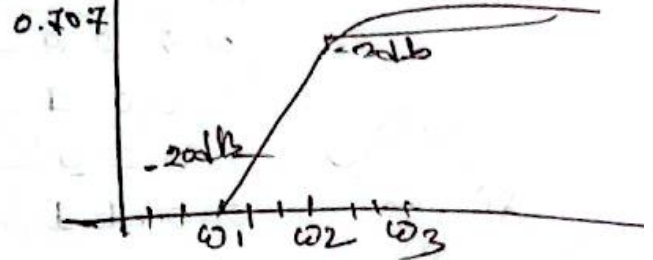


$$f_c = 10 \text{ kHz}$$

$$C = 0.02 \text{ nF}$$

$$R = ?$$

০১০ এর মান change করলে
slope sharp হবে

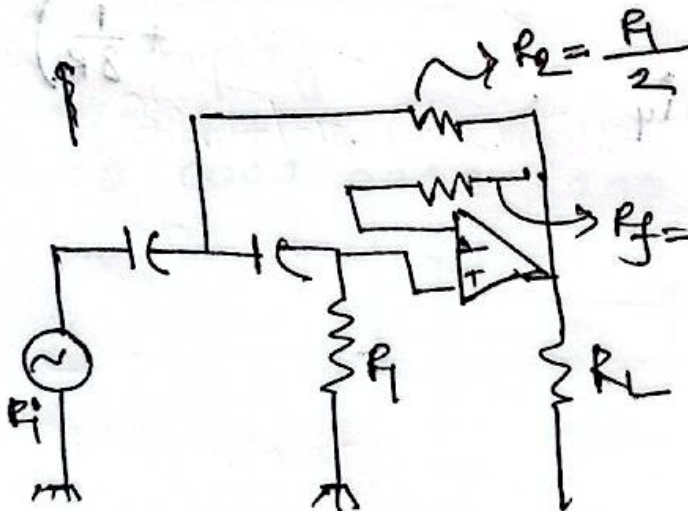R এর value খুব কমে circuit
draw করতে বলা just circuit
R এর value কমানো লাগবে।




High pass
filter with a
roll-off of -40dB
diode

19.01.26

Digital - Analog
Analog - Digital

b_0	b_1	b_2	b_3	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	

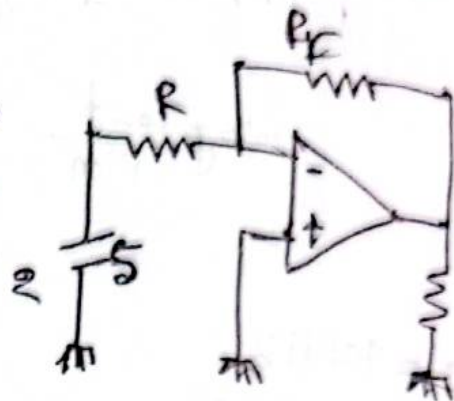

$$\begin{aligned}
 V_o &= -\frac{R_F}{R} \times 5 \\
 &= -\frac{R}{4R} \times 5 \\
 &= -\frac{5}{4}
 \end{aligned}$$


$$V_o = -\frac{R}{2R} \times 5$$

$$V_o = -V_{in} \times R_F \left(\frac{1}{R} + \frac{1}{2R} + \frac{1}{4R} + \frac{1}{8R} \right)$$

$$i = i_1 + i_2 + i_3 + i_4$$

$$i_1 = \frac{V_{in}}{8R}$$


Weighted Register DAC

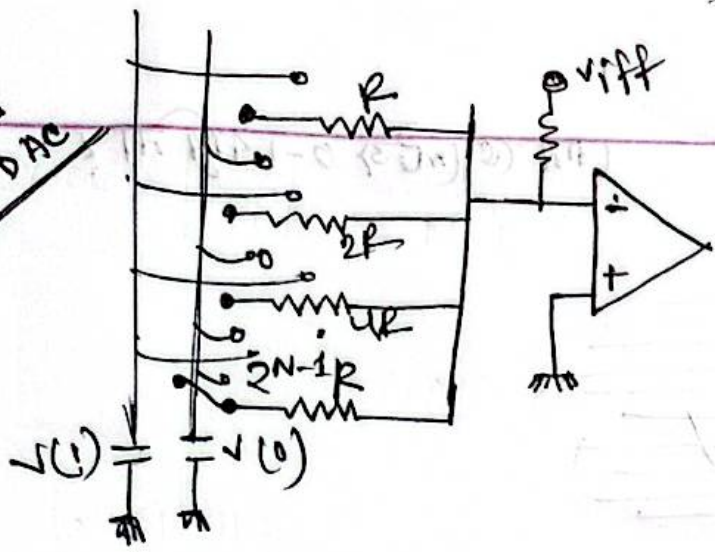

- 0 0 0
- 0 0 1
- 0 1 0
- 0 1 1
- 1 0 0
- 1 0 1
- 1 1 0
- 1 1 1

* Fuzzil Logic

*

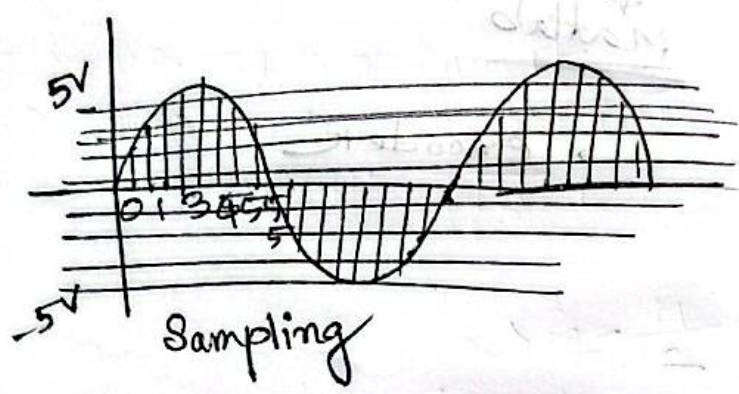

0000 0001 0011 0100

*

